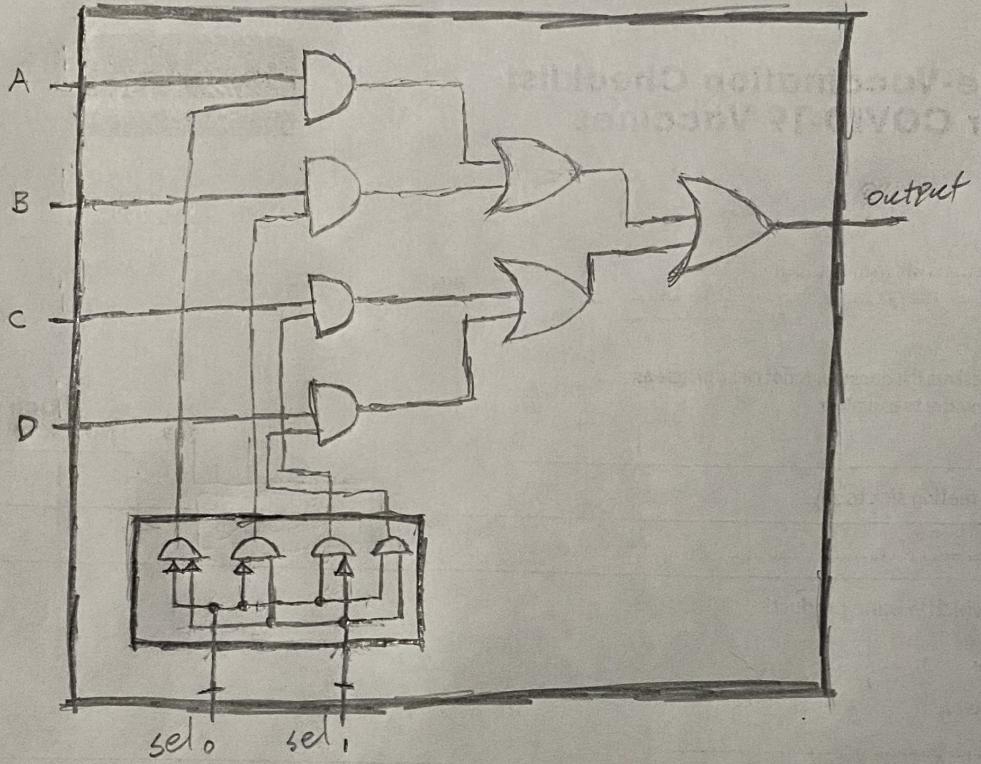


Assignment. 1

Mingzhan Liu

#1



#2

$$F_1 = (\bar{x}_0 \cdot x_1 \cdot x_2) + (x_0 \cdot \bar{x}_1 \cdot x_2) + (x_0 \cdot x_1 \cdot \bar{x}_2)$$

$$F_2 = (\bar{x}_0 \cdot \bar{x}_1 \cdot x_2) + (\bar{x}_0 \cdot x_1 \cdot \bar{x}_2) + (x_0 \cdot \bar{x}_1 \cdot \bar{x}_2)$$

$$F_3 = (\bar{x}_0 \cdot \bar{x}_1 \cdot \bar{x}_2) + (\bar{x}_0 \cdot \bar{x}_1 \cdot x_2) + (\bar{x}_0 \cdot x_1 \cdot \bar{x}_2) + (\bar{x}_0 \cdot x_1 \cdot x_2)$$

$$F_4 = (x_0 \cdot \bar{x}_1 \cdot \bar{x}_2) + (x_0 \cdot \bar{x}_1 \cdot x_2) + (x_0 \cdot x_1 \cdot \bar{x}_2) + (x_0 \cdot x_1 \cdot x_2)$$

x_0	x_1	x_2	F_1	F_2	F_3	F_4	x_0
0	0	0	0 0	1	0 0	0	0
0	0	1	0 1	1	0 1	1	0 1
0	1	0	0 1	1	1 0	1	0 1
0	1	1	1 0	1	1 0	1	0 0
1	0	0	0 1	0	1 1	0	1 1
1	0	1	1 0	0	0 0	1	1 0
1	1	1	0 0	0	0 1	1	1 1


$$F_2 \text{ XOR} = x_0 \oplus (x_1 \oplus x_2)$$

$$F_2 \text{ XOR} = (\bar{x}_0 \cdot \bar{x}_1 \cdot x_2) + (\bar{x}_0 \cdot x_1 \cdot \bar{x}_2) + (x_0 \cdot \bar{x}_1 \cdot \bar{x}_2) + (x_0 \cdot x_1 \cdot x_2)$$

#3

$$E = ((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot (\overline{A} + \overline{B} \cdot C)$$


↓

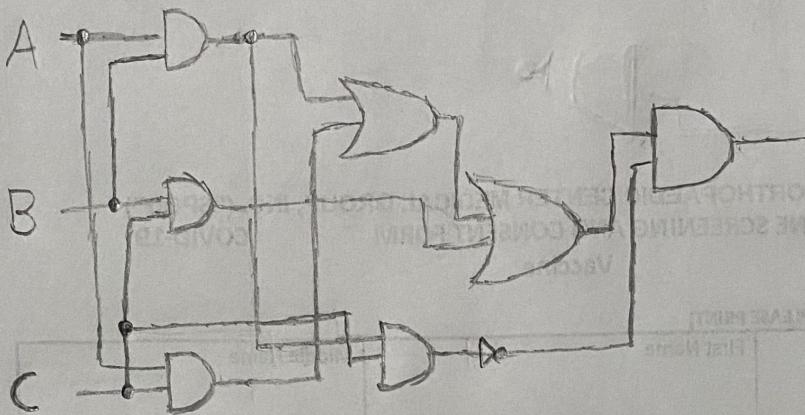

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$E = (A \cdot B \cdot \overline{C}) + (A \cdot \overline{B} \cdot C) + (\overline{A} \cdot B \cdot C)$$

↓

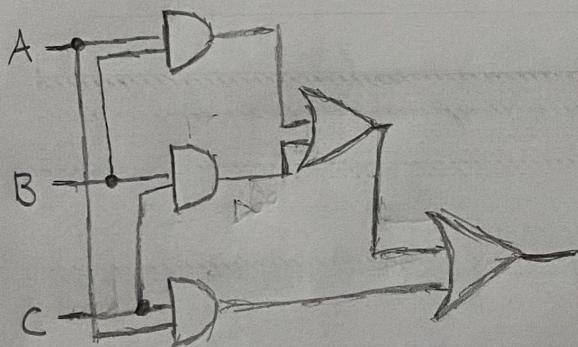

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Equation 2 is more efficient in terms of 2-input gates as it only require 5 gates. While Equation 1 require 7 gates.

4

$$\begin{aligned}
 E &= ((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot (\overline{A \cdot B \cdot C}) \\
 &= ((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot (\overline{A} + \overline{B} + \overline{C}) \\
 &= [(A \cdot B) \cdot (\overline{A} + \overline{B} + \overline{C})] + [A \cdot C) \cdot (\overline{A} + \overline{B} + \overline{C})] \\
 &\quad + [(B \cdot C) \cdot (\overline{A} + \overline{B} + \overline{C})] \\
 &= [\overline{(A \cdot B \cdot A)} + (A \cdot B \cdot \overline{B}) + (A \cdot B \cdot \overline{C})] + \\
 &\quad [\overline{(A \cdot C \cdot A)} + (A \cdot C \cdot \overline{B}) + (A \cdot C \cdot \overline{C})] + \\
 &\quad [\overline{(B \cdot C \cdot A)} + (B \cdot C \cdot \overline{B}) + (B \cdot C \cdot \overline{C})] \\
 &= [(\emptyset) + (A \cdot \emptyset) + (A \cdot B \cdot \overline{C})] + \\
 &\quad [(\emptyset) + (A \cdot \overline{B} \cdot \emptyset) + (A \cdot \emptyset)] + \\
 &\quad [(\emptyset) + (C \cdot \overline{A}) + (C \cdot \emptyset) + (B \cdot \emptyset)] \\
 &= [A \cdot B \cdot \overline{C}] + (A \cdot C \cdot \overline{B}) + (B \cdot C \cdot \overline{A}) \\
 &= \underline{(A \cdot B \cdot \overline{C}) + (A \cdot \overline{B} \cdot C) + (\overline{A} \cdot B \cdot C)} - \text{Basic laws} \\
 &\quad A \cdot \overline{A} = \emptyset \\
 &\quad A \cdot \emptyset = \emptyset \\
 &\quad \text{Associative laws}
 \end{aligned}$$

Therefore :

$$\underline{((A \cdot B) + (A \cdot C) + (B \cdot C)) \cdot (\overline{A \cdot B \cdot C})} \equiv (A \cdot B \cdot \overline{C}) + (A \cdot \overline{B} \cdot C) + (\overline{A} \cdot B \cdot C)$$

5

$$\begin{aligned}
 \text{XOR} &= (A + B) \cdot \overline{(A \cdot B)} \\
 &= (A + B) \cdot (\overline{A} + \overline{B}) \\
 &= (A \cdot (\overline{A} + \overline{B})) + (B \cdot (\overline{A} + \overline{B})) \\
 &= [(A \cdot \overline{A}) + (A \cdot \overline{B})] + [(B \cdot \overline{A}) + (B \cdot \overline{B})] \\
 &= [\emptyset + (A \cdot \overline{B})] + [(B \cdot \overline{A}) + \emptyset] \\
 &= (A \cdot \overline{B}) + (B \cdot \overline{A}) \\
 &= \underline{(A \cdot \overline{B}) + (\overline{A} \cdot B)} \\
 &\quad - \text{DeMorgan's laws} \\
 &\quad - \text{Distributive laws} \\
 &\quad - \text{Distributive laws} \\
 &\quad - \text{basic laws } \overline{A} \cdot A = \emptyset \\
 &\quad - \text{basic laws } A + 0 = A \\
 &\quad - \text{commutative laws}
 \end{aligned}$$

Therefore :

$$\underline{(A + B) \cdot (\overline{A \cdot B})} \equiv (A \cdot \overline{B}) + (\overline{A} \cdot B)$$

#6

3 - input XOR

A	B	C	Output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$3 \text{XOR} = (\bar{A} \cdot \bar{B} \cdot C) + (\bar{A} \cdot B \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot B \cdot C)$$

